

Find the average power absorbed/supplied by each element in the following circuits:

